

Principles Of Digital Design

Flip-Flops


Clocks

Latches

Flip-flops

State diagrams


Topic preview

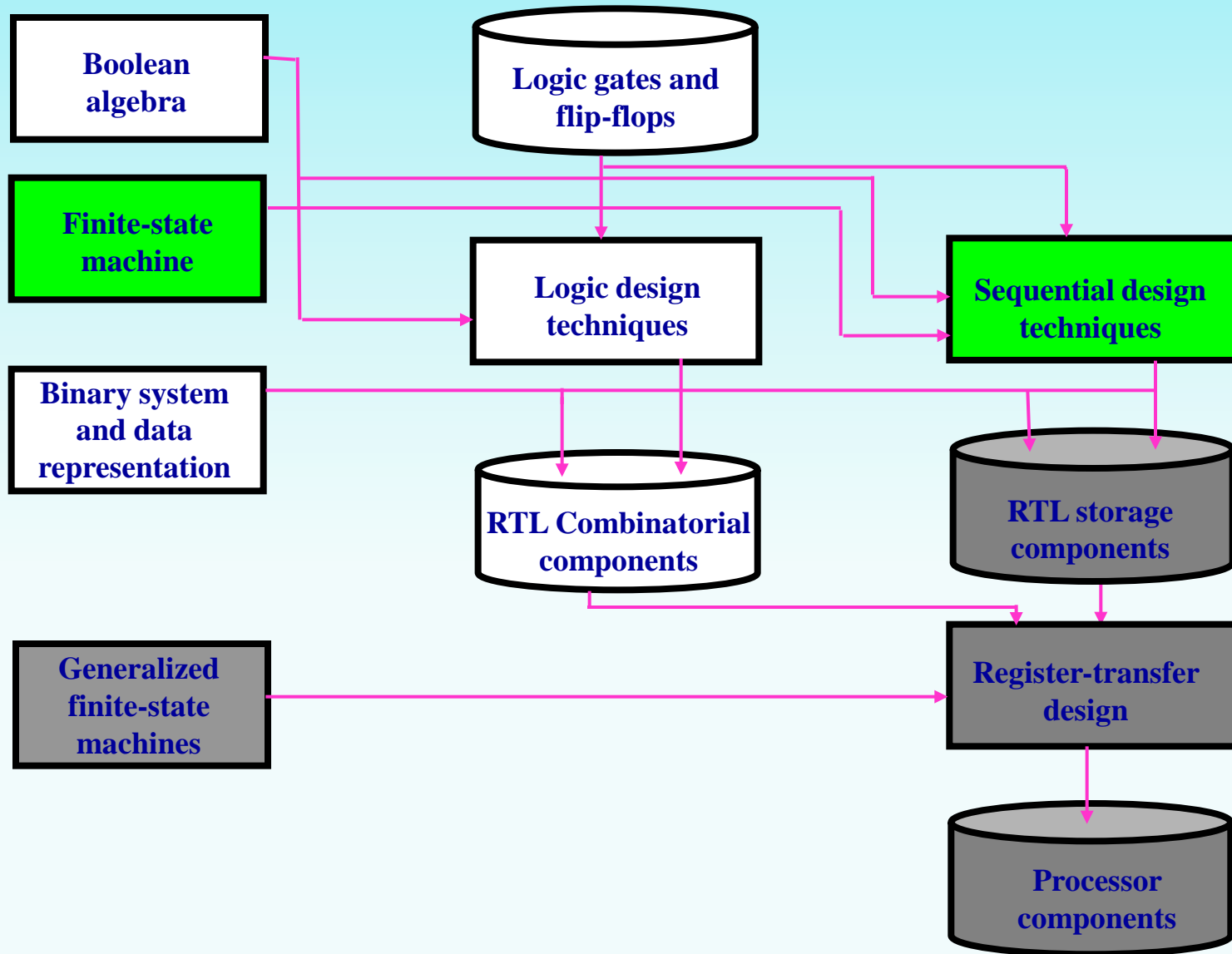

Sequential components

- Sequential components contain memory elements
- The output values of sequential components depend on the input values and the values stored in the memory elements
- The values in the memory elements define the state of sequential components
- Example : Ring counter that starts the answering machine after 4 rings
- Sequential components can be
(1) asynchronous or (2) synchronous
- Asynchronous sequential components change their state and output values as a response to change in input values
- Synchronous sequential components change their state and output values at fixed points of time defined by the clock signal


Clock signal

 

- **Clock period** (measured in micro, nano seconds) is the time between successive transitions in the same direction
- **Clock frequency** (measured in MHz, GHz) is the reciprocal of clock period
- **Clock width** is the time interval during which clock is equal to 1
- **Duty cycle** is the ratio of the clock width and clock period
- **Clock signal is active high** if the changes occur at the rising edge or during the clock width
- **Clock signal is active low** otherwise

SR-latch (NOR implementation)

 
- SR-latch has two states: (1) set state ($Q=1$) and (2) reset state ($Q=0$)



Logic schematic

S	R	Q	$Q (next)$	$Q' (next)$
0	0	0	0	1 (hold)
0	0	1	1	0 (hold)
0	1	X	0	1 (reset)
1	0	X	1	0 (set)
1	1	X	0	0 (?)


Truth table

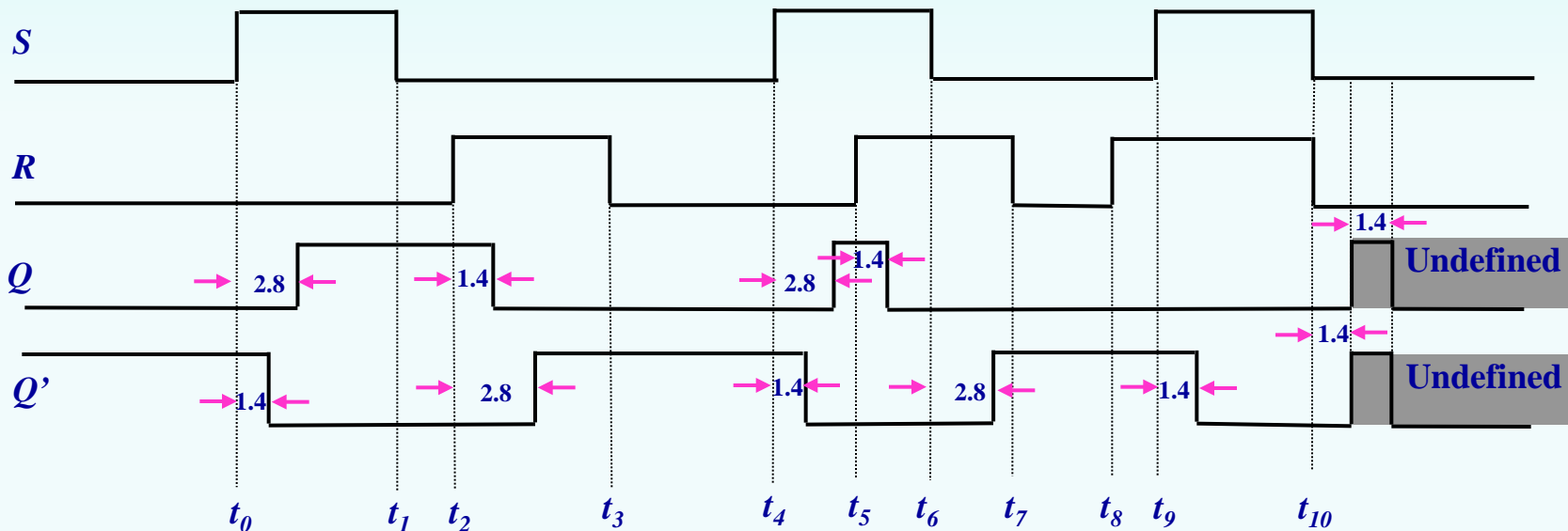


Timing diagram

Gated SR-latch

- Control signal C activates the latch

 


Graphic symbol

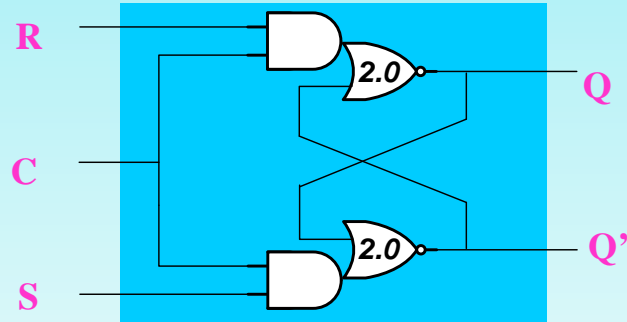

Logic schematic


C	S	R	Q	Q(next)	
0	X	X	0	0	(inactive)
0	X	X	1	1	(inactive)
1	0	0	0	0	(hold)
1	0	0	1	1	(hold)
1	0	1	X	0	(reset)
1	1	0	X	1	(set)
1	1	1	X	NA	(?)

Truth table

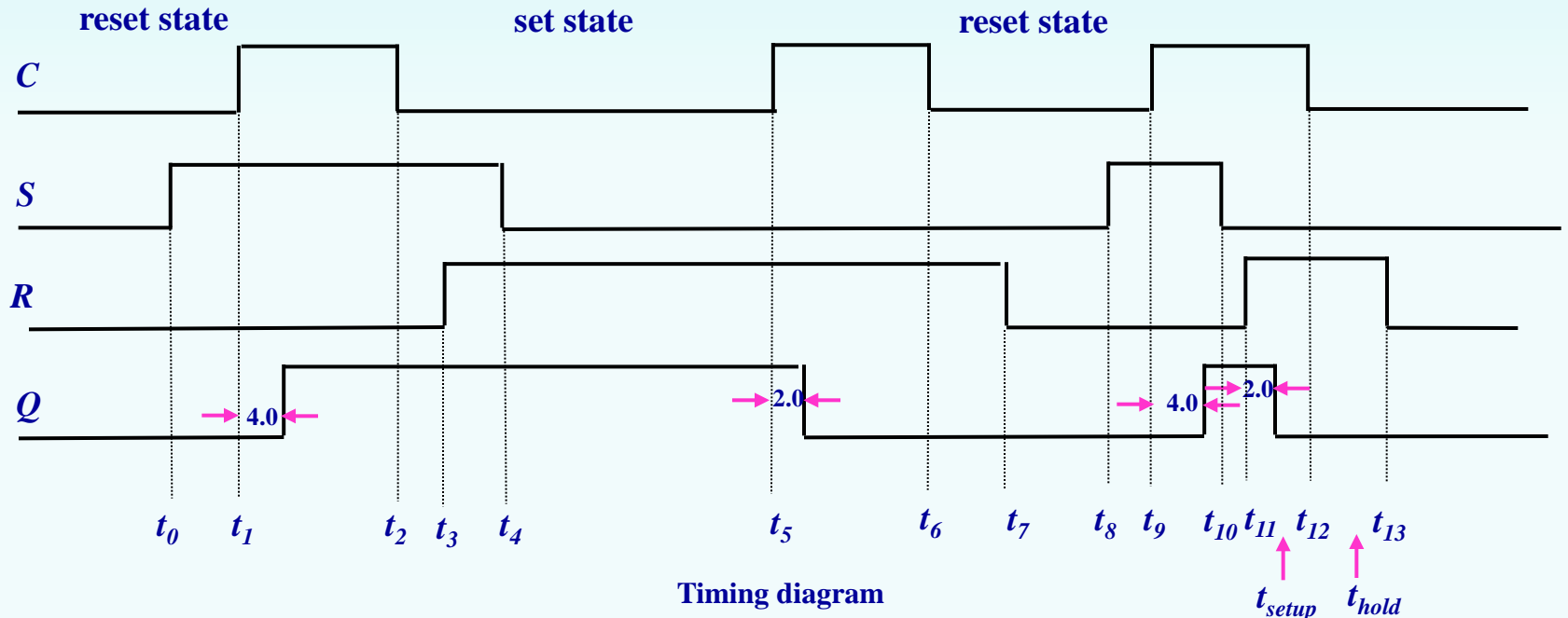


Timing diagram

Gated D-latch

 


Graphic symbol

 

Logic schematic

C	D	Q	$Q(next)$
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

Truth table

 

Timing diagram


- Setup time is minimum time inputs must be stable before $C \downarrow$
- Hold time is minimum time inputs must be stable after $C \downarrow$
- Q follows D while C is asserted as long as D satisfies setup and hold time restrictions

Flip Flops


- Latches are level-sensitive since they respond to input changes during clock width.
- **Latches are difficult to work with for this reason.**
- Flip-Flops respond to input changes only during the change in clock signal.
- **They are easy to work with though more expensive than latches.**
- **Several styles of flip-flops are available.**
 - (1) master-slave (MS)
 - (2) edge-triggered (ET)
 - (3) ...

Erroneous shifting with D-latches

 - Erroneous operation is possible with level-sensitive latches



Logic schematic

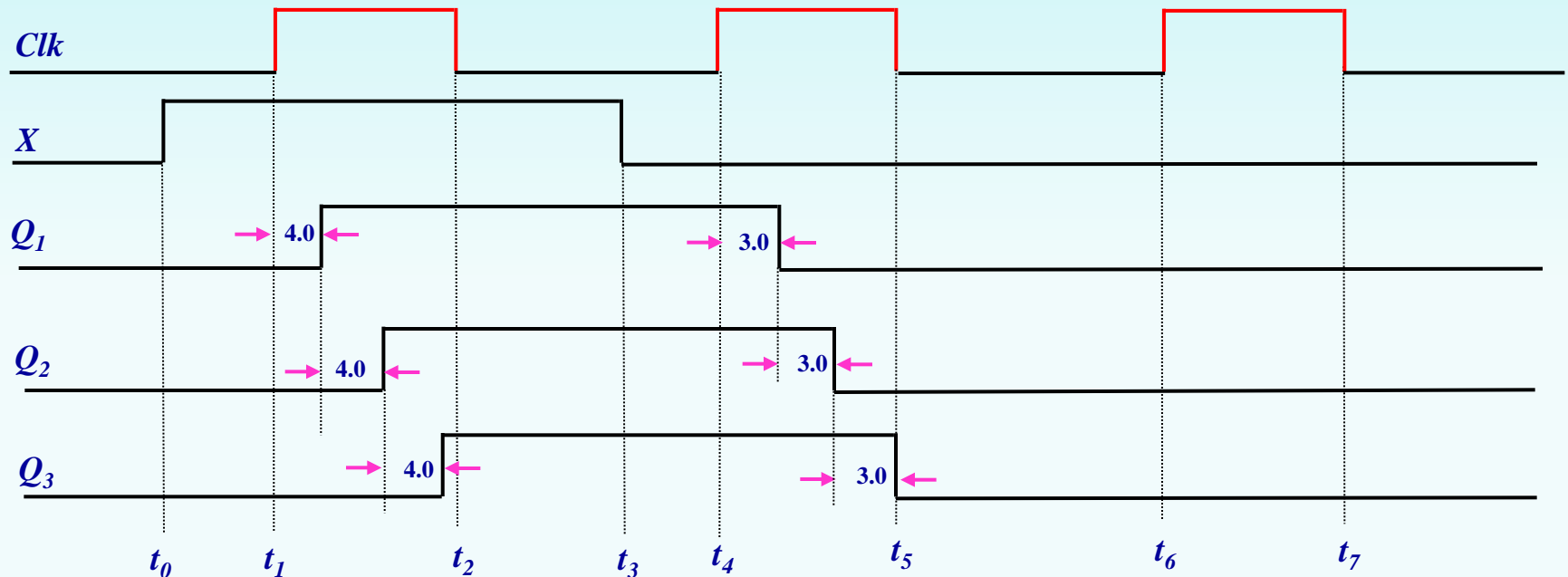


Timing diagram


Note: Low-to-high delay is 4.0ns. High-to-low delay is 3.0ns.

Master-slave flip-flop

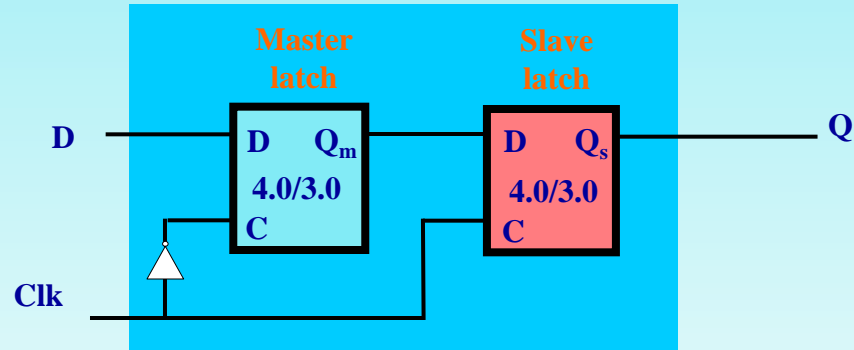• In a MS flip-flop D is sampled and stored at the rising edge (low-to-high) of the Clk signal




Logic schematic

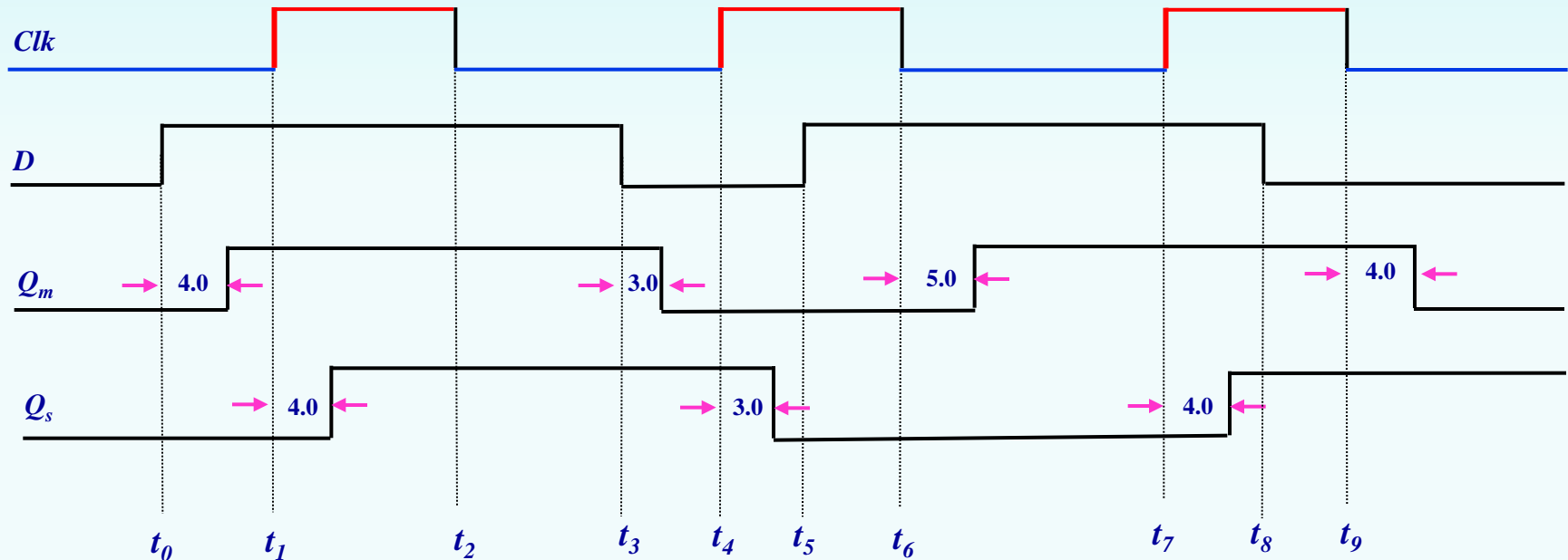


Timing diagram

Shifting with master-slave flip-flops

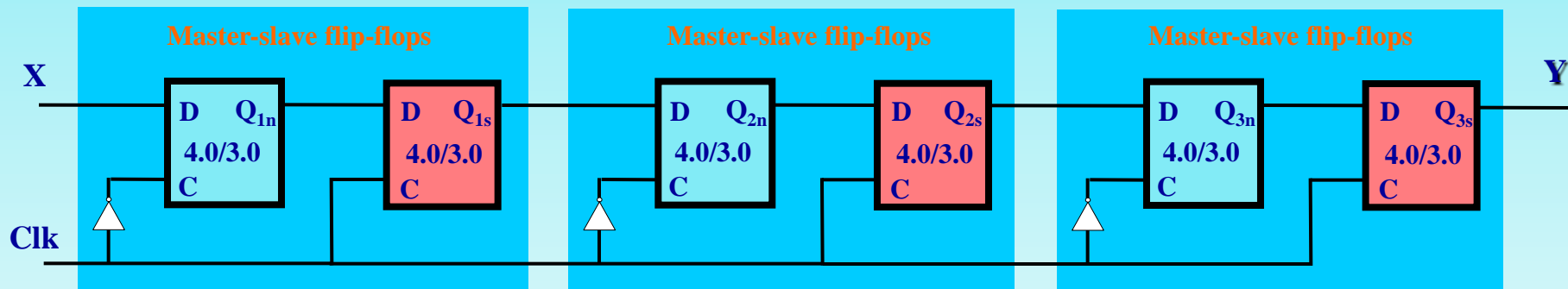

Logic schematic

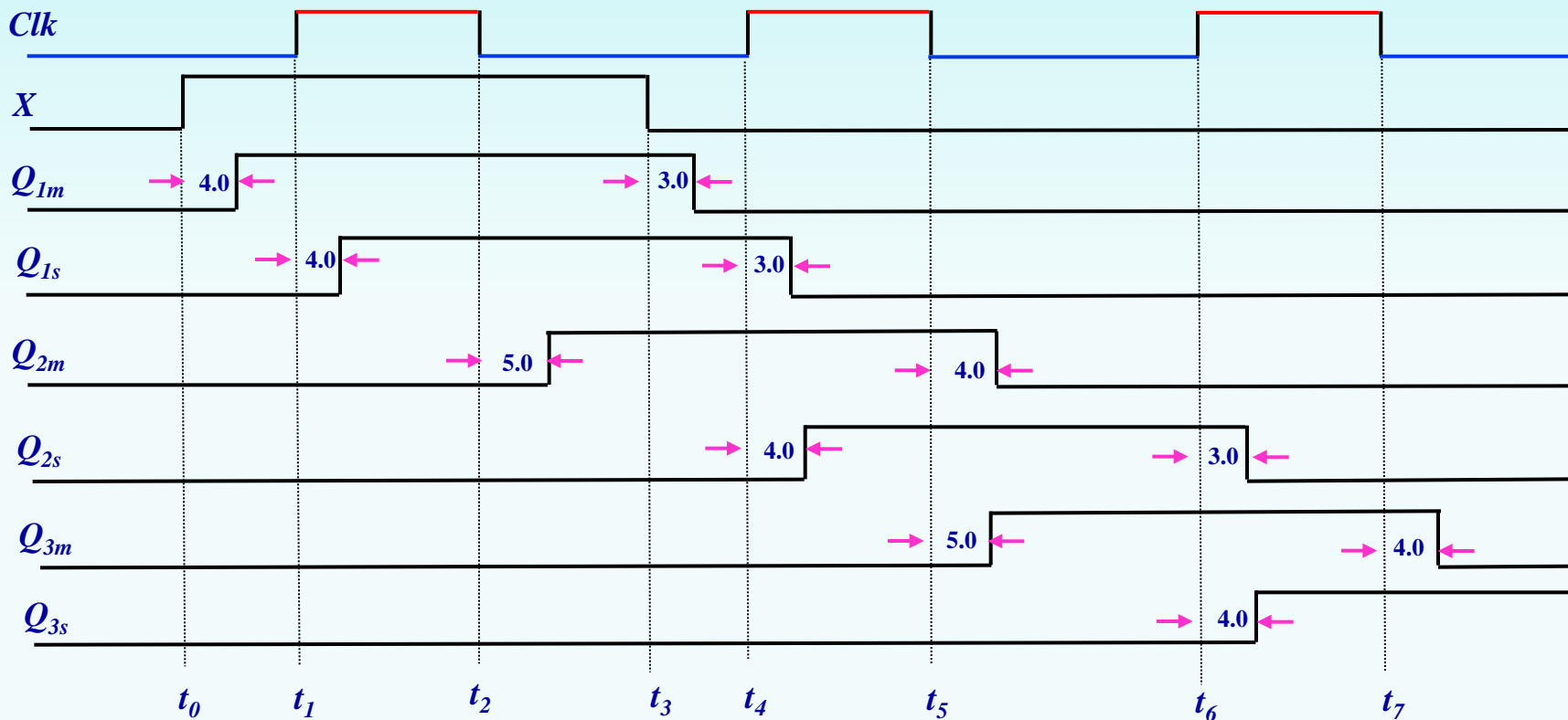


Timing diagram

Flip-flop types


Flip-flop name	Flip-flop symbol	Characteristic table	Characteristic equation	Excitation table																																			
SR		<table border="1"> <thead> <tr> <th>S</th> <th>R</th> <th>$Q(next)$</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>Q</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>NA</td> </tr> </tbody> </table>	S	R	$Q(next)$	0	0	Q	0	1	0	1	0	1	1	1	NA	$Q(next) = S + R'Q$ $SR = 0$	<table border="1"> <thead> <tr> <th>Q</th> <th>$Q(next)$</th> <th>S</th> <th>R</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	Q	$Q(next)$	S	R	0	0	0	X	0	1	1	0	1	0	0	1	1	1	X	0
S	R	$Q(next)$																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	NA																																					
Q	$Q(next)$	S	R																																				
0	0	0	X																																				
0	1	1	0																																				
1	0	0	1																																				
1	1	X	0																																				
	State diagram																																						
D		<table border="1"> <thead> <tr> <th>D</th> <th>$Q(next)$</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> </tr> </tbody> </table>	D	$Q(next)$	0	0	1	1	$Q(next) = D$	<table border="1"> <thead> <tr> <th>Q</th> <th>$Q(next)$</th> <th>D</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	Q	$Q(next)$	D	0	0	0	0	1	1	1	0	0	1	1	1														
D	$Q(next)$																																						
0	0																																						
1	1																																						
Q	$Q(next)$	D																																					
0	0	0																																					
0	1	1																																					
1	0	0																																					
1	1	1																																					
	State diagram																																						

Note: For master-slave flip-flops data inputs must satisfy set-up and hold time constraints.

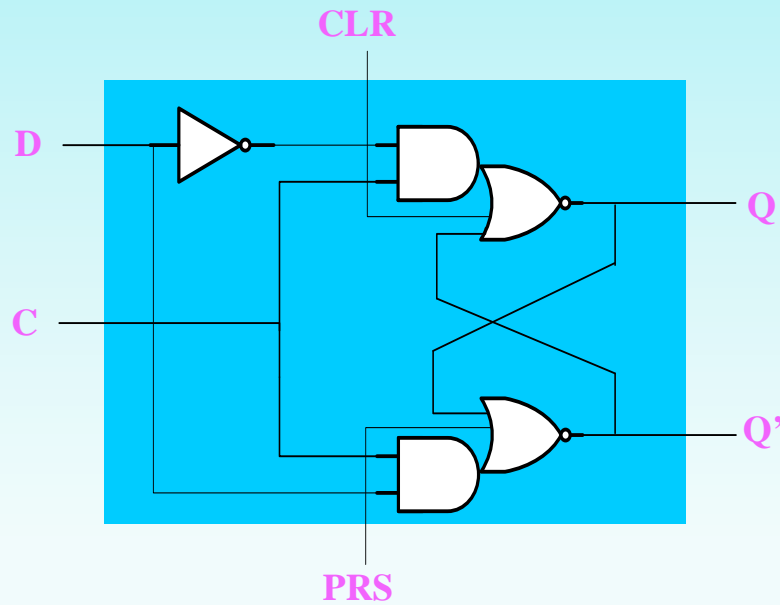A latch / flip-flop with asynchronous inputs



D latch

 

Graphic symbol

Summary

- We introduced memory elements
 - ◆ Latches (asynchronous)
 - ◆ Flip-flops (synchronous)
- We presented several ways to describe memory elements
 - ◆ Characteristic tables
 - ◆ Characteristic equations
 - ◆ State diagrams
 - ◆ Timing diagrams
- We introduced the concept of a state diagram >> FSM